

# COL215P Assignment 1

Gunjan Kumar - 2019CS10353


T Abishek - 2019CS10407

## Introduction

- We implemented the logical AND gate IN VHDL and simulated it using a test bench. Then, we synthesised and implemented this on the BASYS3 FPGA board by loading the bit code into it.


## Observations

- Simulation Result:

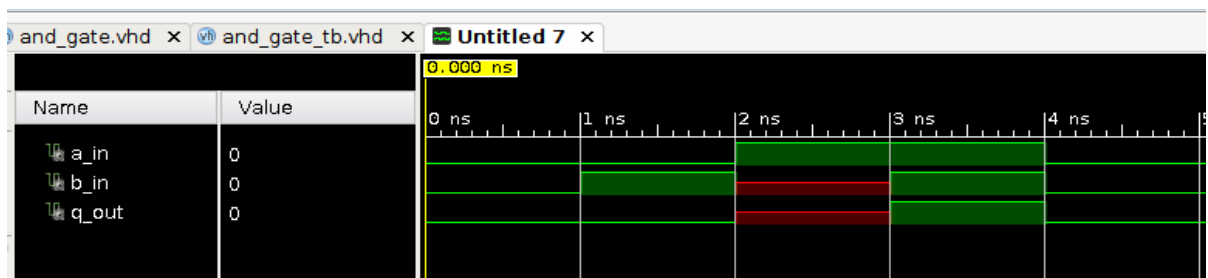

This is an implementation of AND gate. So, if a is 0 and b is 0 then q is 0. If a is 0 and b is 1, then q is 0. If both a and b are 1 then q is 1. If a is 1 and b is X then q is dependent on b and thus, q is X.

 - Schematic Diagram obtained after Synthesis:




- Resource Utilisation:

Hierarchy			
	Name	1	
		Slice LUTs (20800)	Bonded IOB (106)
	and_gate	1	3


Number of LUTs used = 1  
Number of BRAM used = 0

Number of Flip-Flop used = 0  
Number of IOB used = 3


- Implementation on FPGA board:

 


SW0(a) is on and SW1(b) is on

 

SW0(a) is on and SW1(b) is off

 

SW0(a) is off and SW1(b) is on

 

SW0(a) is off and SW1(b) is off